

SERIES & PARALLEL RESISTORS

OBJECTIVE

To explore the relationship between voltage and current in networks of resistors connected in series and parallel. By the end of the lab you should have constructed **five** simple circuits.

PROCEDURE

Step 1:

- a) Construct a circuit with two - 1 k Ω resistor in parallel.
 - Record the current through, and voltage across, each resistor as well as the entire network.
 - Using the ohmmeter, measure the equivalent resistance of the resistor's network.
- b) Repeat for the two - 1 k Ω resistor in series.

Step 2:

It is possible to construct several networks containing series and/or parallel combinations of resistors that all have the same equivalent resistance.

- a) Construct a network with a total resistance of 250 Ω from two 1 k Ω resistors and one 500 Ω resistor
 - Using the ohmmeter, measure the equivalent resistance of the resistor's network.
 - Record the current through and voltage across each resistor, as well as the entire network.
- b) Construct a network with a total resistance of 250 Ω from three 500 Ω resistors and one 1 k Ω resistor. Repeat your measurements.

Step 3:

Construct a network with a total resistance of 1 k Ω from two 1 k Ω resistors and one 500 Ω resistor. Repeat your measurements.

GRAPHS AND DIAGRAMS

Make schematic diagrams of each configuration.


QUESTIONS AND CALCULATIONS

For each configuration:

1. **Using the given values of the resistors**, compute the theoretical equivalent resistance. **Compare** the measured value obtained with the ohmmeter to that theoretical equivalent resistance.
2. **Using Ohm's law**, verify that the measured currents and voltages matches the given values of each resistors, as well as the theoretical equivalent resistance.

Last name: First name:

DATA SHEETS

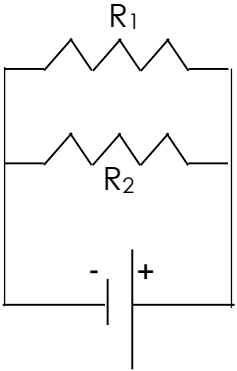Step 1 a) two - 1 kΩ resistor in parallel																			
<p style="text-align: center;">Circuit diagram:</p>  <p style="text-align: center; margin-top: 20px;"> $R_1 = 1\text{ k}\Omega$ $R_2 = 1\text{ k}\Omega$ </p>	<table border="1" style="width: 100%; border-collapse: collapse; margin-bottom: 20px;"> <thead> <tr> <th style="width: 20%;"></th> <th style="width: 30%;">Current (mA)</th> <th style="width: 50%;">Voltage (V)</th> </tr> </thead> <tbody> <tr> <td style="text-align: center;">R₁</td> <td></td> <td></td> </tr> <tr> <td style="text-align: center;">R₂</td> <td></td> <td></td> </tr> <tr> <td style="text-align: center;">Battery</td> <td></td> <td></td> </tr> </tbody> </table> <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 20%;"></th> <th style="width: 30%;">Given value</th> <th style="width: 50%;">Measured value</th> </tr> </thead> <tbody> <tr> <td style="text-align: center;">R_{eq} (Ω)</td> <td style="text-align: center;">500</td> <td></td> </tr> </tbody> </table>		Current (mA)	Voltage (V)	R ₁			R ₂			Battery				Given value	Measured value	R _{eq} (Ω)	500	
	Current (mA)	Voltage (V)																	
R ₁																			
R ₂																			
Battery																			
	Given value	Measured value																	
R _{eq} (Ω)	500																		

Step 1 b) two - 1 kΩ resistor in series																			
<p style="text-align: center;">Circuit diagram:</p> <p style="text-align: center; margin-top: 20px;"> $R_1 = 1\text{ k}\Omega$ $R_2 = 1\text{ k}\Omega$ </p>	<table border="1" style="width: 100%; border-collapse: collapse; margin-bottom: 20px;"> <thead> <tr> <th style="width: 20%;"></th> <th style="width: 30%;">Current (mA)</th> <th style="width: 50%;">Voltage (V)</th> </tr> </thead> <tbody> <tr> <td style="text-align: center;">R₁</td> <td></td> <td></td> </tr> <tr> <td style="text-align: center;">R₂</td> <td></td> <td></td> </tr> <tr> <td style="text-align: center;">Battery</td> <td></td> <td></td> </tr> </tbody> </table> <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 20%;"></th> <th style="width: 30%;">Given value</th> <th style="width: 50%;">Measured value</th> </tr> </thead> <tbody> <tr> <td style="text-align: center;">R_{eq} (Ω)</td> <td style="text-align: center;">2000</td> <td></td> </tr> </tbody> </table>		Current (mA)	Voltage (V)	R ₁			R ₂			Battery				Given value	Measured value	R _{eq} (Ω)	2000	
	Current (mA)	Voltage (V)																	
R ₁																			
R ₂																			
Battery																			
	Given value	Measured value																	
R _{eq} (Ω)	2000																		

Last name: First name:

Step 2 a) two 1 kΩ resistors and one 500 Ω resistor

Circuit diagram:

	Current (mA)	Voltage (V)
R ₁		
R ₂		
R ₃		
Battery		

	Given value	Measured value
R _{eq} (Ω)	250	

R₁ = 1 kΩ

R₂ = 1 kΩ

R₃ = 500 Ω

Step 2 b) one 1 kΩ resistor and three 500 Ω resistors

Circuit diagram:

	Current (mA)	Voltage (V)
R ₁		
R ₂		
R ₃		
R ₄		
Battery		

	Given value	Measured value
R _{eq} (Ω)	250	

R₁ = 1 kΩ

R₂ = 500 Ω

R₃ = 500 Ω

R₄ = 500 Ω

Last name: First name:

Step 3 two 1 k Ω resistors and one 500 Ω resistor

Circuit diagram:

	Current (mA)	Voltage (V)
R ₁		
R ₂		
R ₃		
Battery		

	Given value	Measured value
R _{eq} (Ω)	1000	

R₁ = 1 k Ω

R₂ = 1 k Ω

R₃ = 500 Ω